

# Topic 11

## Examples

國立高雄大學電機工程學系


陳春僥

[cychen@ieee.org](mailto:cychen@ieee.org)

June 13, 2019


1

## Seven-Segment LED Controller

 

```
module Seven_Seg_Display ( output reg [6: 0] Display, input [3: 0] BCD);
    // abc_defg
    parameter BLANK      = 7'b111_1111;
    parameter ZERO       = 7'b000_0001; // h01
    parameter ONE        = 7'b100_1111; // h4f
    parameter TWO        = 7'b001_0010; // h12
    parameter THREE      = 7'b000_0110; // h06
    parameter FOUR       = 7'b100_1100; // h4c
    parameter FIVE       = 7'b010_0100; // h24
    parameter SIX        = 7'b010_0000; // h20
    parameter SEVEN      = 7'b000_1111; // h0f
    parameter EIGHT      = 7'b000_0000; // h00
    parameter NINE       = 7'b000_0100; // h04
    always @ (BCD)
    case (BCD)
        0: Display = ZERO;
        1: Display = ONE;
        2: Display = TWO;
        3: Display = THREE;
        4: Display = FOUR;
        5: Display = FIVE;
        6: Display = SIX;
        7: Display = SEVEN;
        8: Display = EIGHT;
        9: Display = NINE;
        default: Display = BLANK;
    endcase
endmodule
```
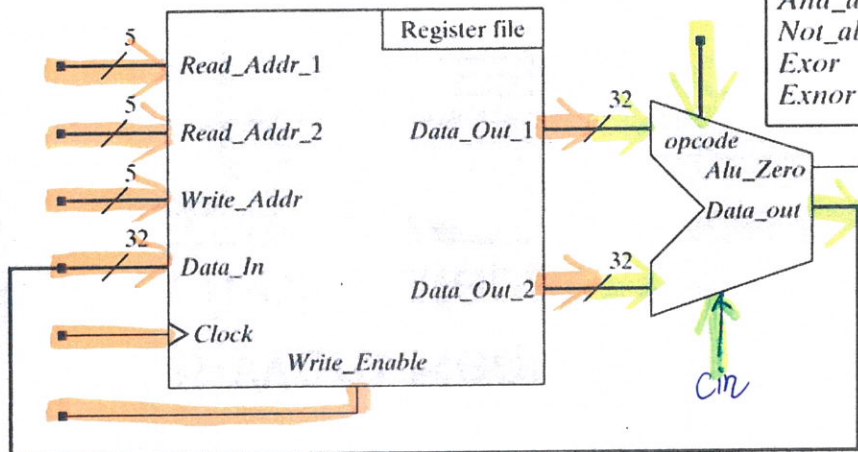
# A 32-Word Register File + an ALU with a 32-bit Datapath



Operand	Function
Add	$a + b + c_{in}$
Subtract	$a + \sim b + c_{in}$
Subtract_a	$b + \sim a + \sim c_{in}$
Or_ab	$\{1'b0, a \mid b\}$
And_ab	$\{1'b0, a \& b\}$
Not_ab	$\{1'b0, (\sim a) \& b\}$
Exor	$\{1'b0, a \wedge b\}$
Exnor	$\{1'b0, a \sim \wedge b\}$

國立高雄大學電機工程學系 陳春僑

3

# A 8-Word Register File + an ALU with an 8-bit Datapath

1

```

module alu_8b (
  output reg [8:0] alu_out,
  input [7:0] a, b,
  input c_in,
  input [2:0] opcode
);
  parameter [2:0] add = 0;
  parameter [2:0] subtract = 1;
  parameter [2:0] subtract_a = 2;
  parameter [2:0] or_ab = 3;
  parameter [2:0] and_ab = 4;
  parameter [2:0] not_ab = 5;
  parameter [2:0] exor = 6;
  parameter [2:0] exnor = 7;

  always @ (a, b, c_in, opcode)
  case (opcode)
    add: alu_out = a + b + c_in;
    subtract: alu_out = a + (~b) + c_in;
    subtract_a: alu_out = b + (~a) + ~c_in;
    or_ab: alu_out = {1'b0, a | b};
    and_ab: alu_out = {1'b0, a & b};
    not_ab: alu_out = {1'b0, (~a) & b};
    exor: alu_out = {1'b0, a ^ b};
    exnor: alu_out = {1'b0, a ~^ b};
  endcase
endmodule
  
```

Operations  
Assignment

2

```

module t_alu_8b;
  reg [7:0] a, b;
  reg c_in;
  reg [2:0] opcode;
  reg [79:0] ocs;
  wire [8:0] alu_out;
  integer j, k;

  parameter [2:0] add = 0;
  parameter [2:0] subtract = 1;
  parameter [2:0] subtract_a = 2;
  parameter [2:0] or_ab = 3;
  parameter [2:0] and_ab = 4;
  parameter [2:0] not_ab = 5;
  parameter [2:0] exor = 6;
  parameter [2:0] exnor = 7;

  parameter [79:0] ocs_0 = "add";
  parameter [79:0] ocs_1 = "subtract";
  parameter [79:0] ocs_3 = "or_ab";
  parameter [79:0] ocs_4 = "and_ab";
  parameter [79:0] ocs_5 = "not_ab";
  parameter [79:0] ocs_6 = "exor";
  parameter [79:0] ocs_7 = "exnor";

  alu_8b M0 (alu_out, a, b, c_in, opcode);
  
```

```

initial #1000 $finish;
initial begin
  #10 a = 8'h55; //0101_0101
  b = 8'haa; //1010_1010
  for (j = 0; j <= 1; j = j + 1)
    for (k = 0; k <= 7; k = k + 1)
      begin
        #10 c_in = j;
        case (k)
          0: opcode = add;
          1: opcode = subtract;
          2: opcode = subtract_a;
          3: opcode = or_ab;
          4: opcode = and_ab;
          5: opcode = not_ab;
          6: opcode = exor;
          7: opcode = exnor;
        endcase
      end
end

always @ (opcode)
case (opcode)
  add: ocs = ocs_0;
  subtract: ocs = ocs_1;
  subtract_a: ocs = ocs_2;
  or_ab: ocs = ocs_3;
  and_ab: ocs = ocs_4;
  not_ab: ocs = ocs_5;
  exor: ocs = ocs_6;
  exnor: ocs = ocs_7;
endcase
endmodule
  
```

依序不同 Operations  
Strings to Assignments


3

國立高雄大學電機工程學系 陳春僑

4


 
# A 8-Word Register File + an ALU with an 8-bit Datapath



國立高雄大學電機工程學系 陳春僑

5

# A 8-Word Register File + an ALU with an 8-bit Datapath

```

module alu_8b_register (
    output [8: 0] alu_out, // Re-sized
    input [7: 0] Data_in,
    input [2: 0] Read_Addr_1, Read_Addr_2, Write_Addr,
    input [2: 0] opcode,
    input Write_Enable, Clock,
    input c_in
);
    wire [7: 0] Data_Out_1, Data_Out_2;

    alu_8b M0_ALU (alu_out, Data_Out_1, Data_Out_2, c_in, opcode);
    Register_File M1_Reg_File (Data_Out_1, Data_Out_2, Data_in, Read_Addr_1,
        Read_Addr_2, Write_Addr, Write_Enable, Clock);
endmodule
    
```

```

module Register_File (
    output [7: 0] Data_Out_1, Data_Out_2,
    input [7: 0] Data_in,
    input [2: 0] Read_Addr_1, Read_Addr_2, Write_Addr,
    input Write_Enable, Clock
);
    reg [7: 0] Reg_File [31: 0]; // 8 x 32 Memory declaration

    assign Data_Out_1 = Reg_File[Read_Addr_1];
    assign Data_Out_2 = Reg_File[Read_Addr_2];

    always @ (posedge Clock) begin
        if (Write_Enable) Reg_File[Write_Addr] <= Data_in;
    end
endmodule
    
```

// Test Plan: Register File  
 // Write to memory with walking ones  
 // Verify read of walking ones from each port

```

module t_Register_File ();
    wire [7: 0] Data_Out_1, Data_Out_2;
    reg [7: 0] Data_in;
    reg [2: 0] Read_Addr_1, Read_Addr_2, Write_Addr;
    reg Write_Enable, Clock;
    integer k;

    Register_File M0(Data_Out_1, Data_Out_2, Data_in,
        Read_Addr_1, Read_Addr_2,
        Write_Addr, Write_Enable, Clock);

    initial #500 $finish;
    initial begin Clock = 0; forever #5 Clock = ~Clock; end
    initial begin
        Data_in = 8'b1000_0000;
        Write_Enable = 1;
        Write_Addr = 0;
        Read_Addr_1 = 0;
        Read_Addr_2 = 0;
        for (k = 0; k <= 31; k = k + 1) begin
            @ (negedge Clock)
            if (Data_in == 8'b1000_0000) Data_in = 8'b0000_0001;
            else Data_in <= Data_in << 1;
            Write_Addr <= Write_Addr + 1;
            Read_Addr_1 <= Read_Addr_1 + 1;
            Read_Addr_2 <= Read_Addr_2 + 1;
        end
    end
endmodule
    
```

負緣讀出 & 更新位址

running 1's

國立高雄大學電機工程學系 陳春僑

6



## HDL Design & Simulation — Topic 11: Examples

4

```
parameter [79: 0] ocs_0 = "add";
parameter [79: 0] ocs_1 = "subtract";
parameter [79: 0] ocs_2 = "subtract_a";
parameter [79: 0] ocs_3 = "or_ab";
parameter [79: 0] ocs_4 = "and_ab";
parameter [79: 0] ocs_5 = "not_ab";
parameter [79: 0] ocs_6 = "exor";
parameter [79: 0] ocs_7 = "exnor";
```

```
alu_8b_register M0 (alu_out, Data_in, Read_Addr_1, Read_Addr_2, Write_Addr, opcode,
Write_Enable, c_in, Clock);
```


5

6

```
always @(opcode)
case (opcode)
add: ocs = ocs_0;
subtract: ocs = ocs_1;
subtract_a: ocs = ocs_2;
or_ab: ocs = ocs_3;
and_ab: ocs = ocs_4;
not_ab: ocs = ocs_5;
exor: ocs = ocs_6;
exnor: ocs = ocs_7;
endcase
endmodule
```

7
 
## HDL Design & Simulation -- Topic 11: Examples



國立高雄大學電機工程學系 陳春僥