

Topic A

Introduction to Verilog HDL

陳春僥

May 20, 2021


1



HDL

- HDL—
 - Hardware Description Language
- Two Popular HDL
 - Verilog HDL
 - Like C, C++
 - VHDL
 - Very High Speed Integrated Circuit Hardware Description Language
 - Like PASCAL

Organization of a Testbench

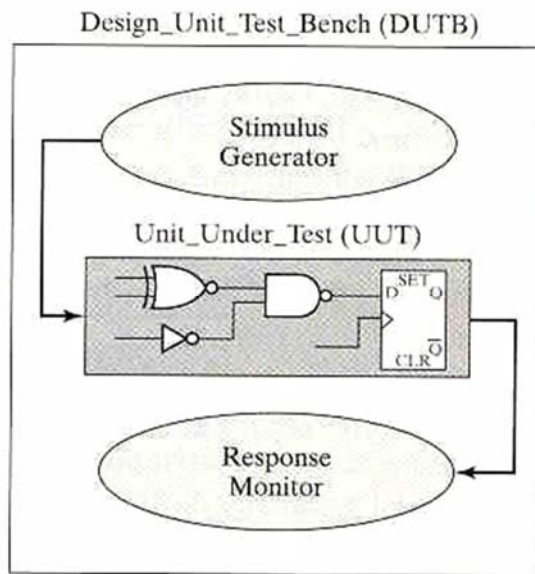

General Form of a Module

```
module module_name [(port_name{, port_name})];  
  
  [input declarations]  
  [output declarations]  
  [inout declarations]  
  
  [wire or tri declarations]  
  [reg or integer declarations]  
  
  [parameter declarations]  
  
  [function or task declarations]  
  [gate instantiations]  
  [module instantiations]  
  [assign continuous assignment]  
  [initial block]  
  [always block]  
  
endmodule
```

Testbench Template

```
module t_DUTB_name ();           // Substitute the name of the UUT
  reg ...;                       // Declaration of register variables
                                // for primary inputs of the UUT
  wire ...;                      // Declaration of primary outputs of the UUT
  parameter                      // Provide a value

  UUT_name M1_instance_name (UUT ports go here);

  initial                        // Develop one or more behaviors for pattern
                                // generation and/or error detection

  begin                          // Behavioral statements generating waveforms
                                // to the input ports, and comments documenting
                                // the test.

  end

  initial $monitor ();           // Specification of signals to be monitored and
                                // displayed as text
  initial #time_out $finish;     // Stopwatch to assure termination of simulation

endmodule
```

A Simple Logic Function


■ Structural Specification

```
module example1 (f, x1, x2, x3);

  input x1, x2, x3;
  output f;

  and (g, x1, x2);
  not (k, x2);
  and (h, k, x3);
  or (f, g, h);


endmodule
```

 

A Simple Logic Function

- Dataflow Specification—
 - Continuous assignment


```
module example3 (f, x1, x2, x3);  
  
  input x1, x2, x3;  
  output f;  
  
  assign f = (x1 & x2) | (~x2 & x3);  
  
endmodule
```

 


A Simple Logic Function

- Behavioral Specification—
 - Procedural assignment
 
```
// Behavioral specification  
module example5 (f, x1, x2, x3);  
  
  input x1, x2, x3;  
  output f;  
  reg f;  
  
  always @ (x1 or x2 or x3)  
    if (x2 == 1)  
      f = x1;  
    else  
      f = x3;  
  
endmodule
```



 

A Simple Logic Function

■ Testbench

```
`timescale 1ns/1ns           // t_unit/t_precision
module t_example1;
  reg x1, x2, x3;
  example1 test (f, x1, x2, x3); // Enter fixture code here
  initial
  begin
    x1 = 1'b0;
    x2 = 1'b0;
    x3 = 1'b0;
    #200
    x1 = 1'b0;
    x2 = 1'b0;
    x3 = 1'b1;
    #200
    x1 = 1'b0;
    x2 = 1'b1;
    x3 = 1'b0;
    #200
    $finish;
  end
endmodule // t_example1
```

```
`timescale 1ns/1ns
module t_example1;
  reg x1, x2, x3;
  example1 test (f, x1, x2, x3); // Enter fixture code here
  initial #600 $stop;
  initial
  begin
    x1 = 1'b0;
    x2 = 1'b0;
    x3 = 1'b0;
    #200
    x1 = 1'b0;
    x2 = 1'b0;
    x3 = 1'b1;
    #200
    x1 = 1'b0;
    x2 = 1'b1;
    x3 = 1'b0;
    #200
  end
endmodule // t_example1
```




Preparing a Testbench

■ Stimulus and design module interaction

Stimulus module

Design module

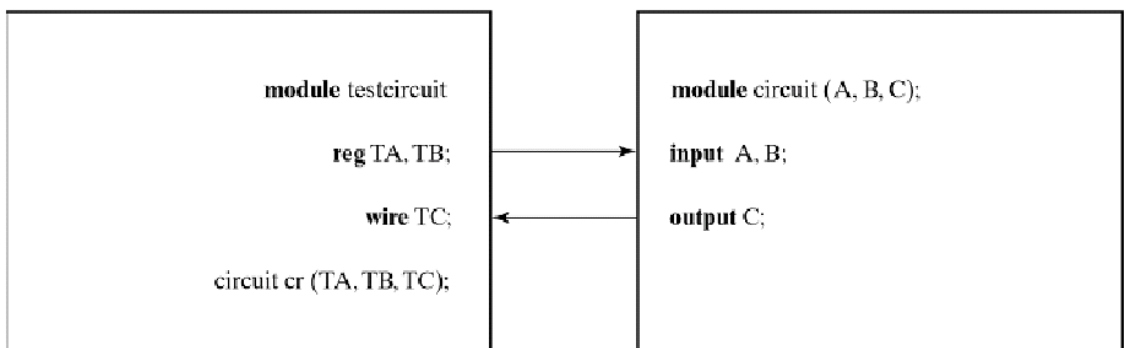



Preparing a Testbench

- System tasks

- `$display`
 - Display one-time value of variables or strings with end-of-line return
- `$write`
 - Same as `$display` but without going to next line
- `$monitor`
 - Display variables whenever a value changes during simulation run
- `$time`
 - Displays simulation time
- `$finish`
 - Terminates the simulation



initial vs. always


- initial—
 - Executed once
 - Good for generating input signals to simulate a design
- always—
 - Executed when the conditions are met

Full Adder

■ Structural Specification (version 1)

```
module fulladd (cout, s, cin, x, y);
  input cin, x, y;
  output cout, s;

   xor (s, cin, x, y);
  and (z1, x, y);
  and (z2, x, cin);
  and (z3, y, cin);
  or (cout, z1, z2, z3);
endmodule
```




Full Adder

■ Structural Specification (version 2)

```
module fulladd(cout, s, cin, x, y);
  input cin, x, y;
  output cout, s;

 
  xor (s, cin, x, y);
  and (z1, x, y),
    (z2, x, cin),
    (z3, y, cin);
  or (cout, z1, z2, z3);
endmodule
```



Full Adder

- Dataflow Specification—
 - Continuous assignment (version 1)


```
module fulladd (cout, s, cin, x, y);  
  
  input cin, x, y;  
  output cout, s;  
  
  assign s = x ^ y ^ cin;  
  assign cout = (x & y) | (x & cin) | (y & cin);  
  
endmodule
```

 

Full Adder

- Dataflow Specification—
 - Continuous assignment (version 2)

```
module fulladd (cout, s, cin, x, y);  
  
  input cin, x, y;  
  output cout, s;  
  
  assign s = x ^ y ^ cin,  
         cout = (x & y) | (x & cin) | (y & cin);  
  
endmodule
```

 

4-Bit Adder

■ Vectored signals

input [3:0] W;

wire [3:1] C;

```
module adder4 (carryout, s, carryin, x, y);
```

```
input carryin;
```

```
input [3:0] x, y;
```

```
output [3:0] s;
```

```
output carryout;
```

```
wire [3:1] c;
```


```
fulladd stage0 (c[1], s[0], carryin, x[0], y[0]);
```

```
fulladd stage1 (c[2], s[1], c[1], x[1], y[1]);
```

```
fulladd stage2 (c[3], s[2], c[2], x[2], y[2]);
```

```
fulladd stage3 (carryout, s[3], c[3], x[3], y[3]);
```

```
endmodule
```

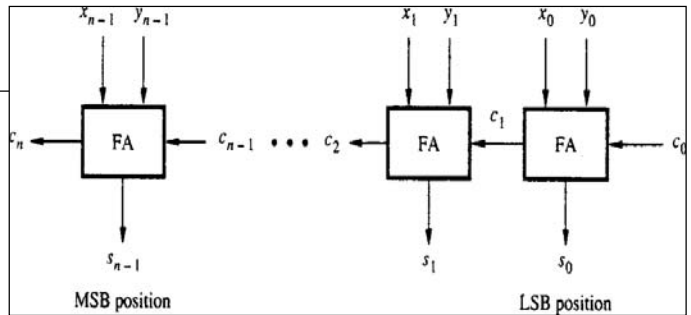

← ordered port connection

n-Bit Adder

■ Parameter

parameter n = 32;

```
module addn (carryout, s, carryin, x, y);
```

```
parameter N = 32;
```

```
input carryin;
```

```
input [N - 1 : 0] x, y;
```

```
output [N - 1 : 0] s;
```

```
output carryout;
```

```
reg [N - 1 : 0] s;
```

```
reg carryout;
```

```
reg [n : 0] c;
```

```
integer k;
```

```
always @(x or y or carryin)
```

```
begin
```

```
  c[0] = carryin;
```

```
  for (k = 0; k < n; k = k + 1)
```

```
  begin
```

```
    s[k] = x[k] ^ y[k] ^ c[k];
```


```
    c[k + 1] = (x[k] & y[k]) | (x[k] & c[k]) | (y[k] & c[k]);
```

```
  end
```

```
  carryout = c[n];
```

```
end
```

```
endmodule
```

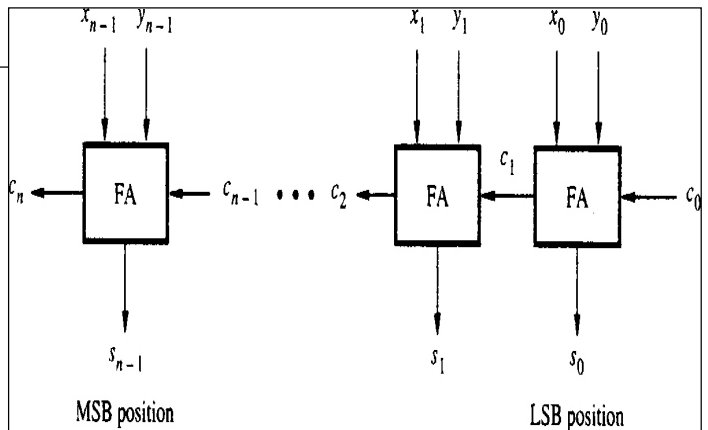

Nets and Variables in Verilog

■ Nets

- wire— default type

```
wire c2, c1, c0;
```

```
wire [2:0] c;
```

■ Variables

- reg
- integer

Full Adder

■ Behavioral Specification—

- Procedural assignment

```
module fulladd (cout, s, cin, x, y);
```


```
  input cin, x, y;
```

```
  output s, cout;
```

```
  reg s, cout;
```

```
  always @(x or y or cin)  
    {cout, s} = x + y + cin;
```

```
endmodule
```

 

n -Bit Adder

- Behavioral Specification—
 - Procedural assignment

```
module addern (s, carryin, x, y);  
  
    parameter N = 32;  
    input carryin;  
    input [N-1 : 0] x, y;  
    output [N-1 : 0] s;  
  
    reg [N-1 : 0] s;  
  
    always @(x or y or carryin)  
        s = x + y + carryin;  
  
endmodule
```

Representation of Numbers in Verilog Code

- Format—
<size_in-bits>'<radix_identifier><significant_digits>
- Examples—

- Fixed-sized

- 12'b100010101001
- 12'b1000_1010_1001
- 12'b1000 1010 1001
- 12'o4251
- 12'h8A9
- 12'd2217

- Unspecified-sized

- 'b100010110
- 'b1_0001_0110
- 'b1 0001 0110
- 'o426
- 'h116
- 278


The Conditional Operator

Syntax—

Conditional_expression ? true_expression : false_expression

 Examples—


```
module mux2to1 (f, w0, w1, s);
    input w0, w1, s;
    output f;
    assign f = s ? w1 : w0;
endmodule
```




(a) Graphical symbol

s	f
0	w ₀
1	w ₁

(b) Truth table

 

(c) Sum-of-products circuit

 


(d) Circuit with transmission gates

23

Chuen-Yau Chen

2-to-1 Multiplexer

 
```
module mux2to1 (f, w0, w1, s);
    input w0, w1, s;
    output f;
    reg f;
    always @(w0 or w1 or s)
        f = s ? w1 : w0;
endmodule
```




(a) Graphical symbol

s	f
0	w ₀
1	w ₁

(b) Truth table

 

(c) Sum-of-products circuit

 


(d) Circuit with transmission gates

24

Chuen-Yau Chen

4-to-1 Multiplexer

 

```

module mux4to1 (f, w0, w1, w2, w3, s);
  input w0, w1, w2, w3;
  input [1 : 0] s;
  output f;

  assign f = s[1] ? (s[0] ? w3 : w2) : (s[0] ? w1 : w0);


endmodule

```

The if-else Statement

- Syntax—
 - if (conditional_expression)
 - statement;
 - else
 - statement;

- Examples—

 

```

module mux2to1 (f, w0, w1, s);

  input w0, w1, s;
  output f;
  reg f;

  always @(w0 or w1 or s)
    if (s == 0)
      f = w0;
    else
      f = w1;

endmodule

```

4-to-1 Multiplexer

```
module mux4to1 (f, w0, w1, w2, w3, s);
```

```
  input w0, w1, w2, w3;
```

```
  input [1:0] s;
```

```
  output f;
```

```
  reg f;
```

```
  always @(w0 or w1 or w2 or w3 or s)
```

```
    if (S == 2'b00)
```

```
      f = w0;
```

```
    else if (s == 2'b01)
```

```
      f = w1;
```


```
    else if (s == 2'b10)
```

```
      f = w2;
```

```
    else if (s == 2'b11)
```

```
      f = w3;
```

```
endmodule
```

 

16-to-1 Multiplexer

```
module mux16to1 (f, w, s16);
```

```
  input [0 : 15] w;
```

```
  input [3 : 0] s16;
```

```
  output f;
```

```
  wire [0 : 3] m;
```

```
  mux4to1 mux1 (m[0], w[0:3], s16[1:0]);
```


```
  mux4to1 mux2 (m[1], w[4:7], s16[1:0]);
```


```
  mux4to1 mux3 (m[2], w[8:11], s16[1:0]);
```

```
  mux4to1 mux4 (m[3], w[12:15], s16[1:0]);
```

```
  mux4to1 mux5 (f, m[0:3], s16[3:2]);
```

```
endmodule
```

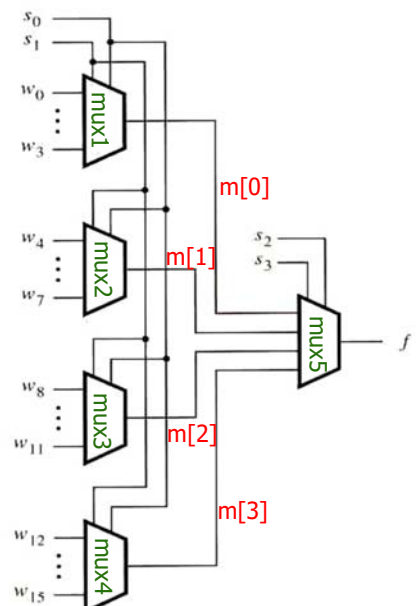

 

The case Statement

■ Syntax—

case (expression)

alternative1: statement;

alternative2: statement;

alternativej: statement;

[**default**: statement;]

endcase



4-to-1 Multiplexer

```
module mux4to1 (f, w, s);
```

```
  input [0 : 3] w;
```

```
  input [1 : 0] s;
```

```
  output f;
```

```
  reg f;
```

```
  always @(w or s)
```

```
    case (s)
```

```
      0: f = w[0];
```


```
      1: f = w[1];
```

```
      2: f = w[2];
```

```
      3: f = w[3];
```

```
    endcase
```

```
endmodule
```

 

2-to-4 Decoder

Example

```

module dec2to4 (y, w, en);

    input [1 : 0] w;
    input en;
    output [0 : 3] y;


    reg [0 : 3] y;

    always @(w or en)
        case ({en, w})
            3'b100: y = 4'b1000;
            3'b101: y = 4'b0100;
            3'b110: y = 4'b0010;
            3'b111: y = 4'b0001;
            default: y = 4'b0000;
        endcase

    endmodule


```

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

 


(a) Truth table

(b) Graphical symbol

 

(c) Logic circuit

2-to-4 Decoder

 

```

module dec2to4 (y, w, en);

```

```

    input [1 : 0] w;
    input en;
    output [0 : 3] y;
    reg [0 : 3] y;

```

```

    always @(w or en)
    begin

```

```

        if (en == 0)
            y == 4'b0000;

```

```

        else
            case (w)
                0: y = 4'b1000;
                1: y = 4'b0100;
                2: y = 4'b0010;
                3: y = 4'b0001;
            endcase

```

```

        end
    end

```

```

endmodule

```


4-to-16 Decoder

```
module dec4to16 (y, w, en);
```

```
    input [3 : 0] w;
```


```
    input en;
```

```
    output [0 : 15] y;
```

```
    wire [0 : 3] m;
```

```
    dec2to4 dec1 (m[0:3], w[3:2], en);
    dec2to4 dec2 (y[0:3], w[1:0], m[0]);
    dec2to4 dec3 (y[4:7], w[1:0], m[1]);
    dec2to4 dec4 (y[8:11], w[1:0], m[2]);
    dec2to4 dec5 (y[12:15], w[1:0], m[3]);
```

```
endmodule
```

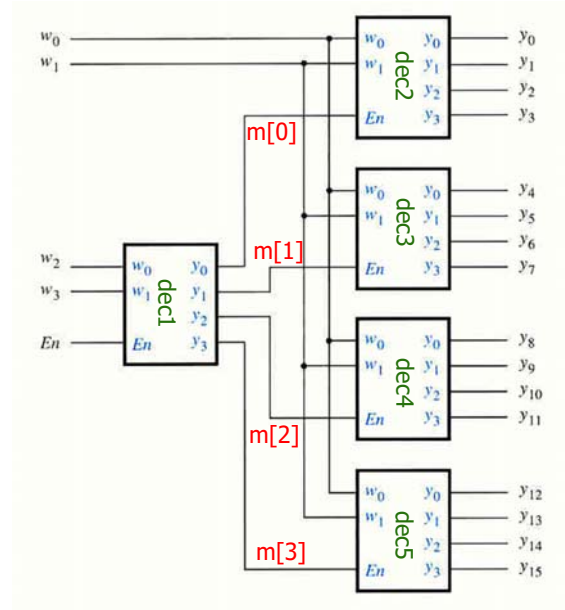

33

BCD-to-7-Segment Display Code Converter

```
module seg7 (leds, bcd);
```

```
    input [3:0] bcd;
```

```
    output [1:7] leds;
```

```
    reg [1:7] leds;
```

```
    always @(bcd)
```

```
        case (bcd) //abcdefg
```

```
0: leds = 7'b11111110;
```

```
1: leds = 7'b01100000;
```

```
2: leds = 7'b1101101;
```

```
3: leds = 7'b1111001;
```

```
4: leds = 7'b0110011;
```

```
5: leds = 7'b1011011;
```

```
6: leds = 7'b1011111;
```

```
7: leds = 7'b1110000;
```


```
8: leds = 7'b1111111;
```

```
9: leds = 7'b1111011;
```


```
default: leds = 7'bx;
```

```
endcase
```

```
endmodule
```

 

(a) Code converter

 

(b) 7-segment display

w ₃	w ₂	w ₁	w ₀	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	0	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

(c) Truth table

34

74381 ALU

Operation	Inputs	Outputs
	$s_2 s_1 s_0$	F
Clear	0 0 0	0 0 0 0
$B - A$	0 0 1	$B - A$
$A - B$	0 1 0	$A - B$
ADD	0 1 1	$A + B$
XOR	1 0 0	$A \text{ XOR } B$
OR	1 0 1	$A \text{ OR } B$
AND	1 1 0	$A \text{ AND } B$
Preset	1 1 1	1 1 1 1

```
//74381 ALU
module alu (f, s, a, b);

    input [2:0] s;
    input [3:0] a, b;
    output [3:0] f;

    reg [3:0] f;

    always @(s or a or b)
        case (s)
            0: f = 4'b0000;
            1: f = b - a;
            2: f = a - b;
            3: f = a + b;
            4: f = a ^ b;
            5: f = a | b;
            6: f = a & b;
            7: f = 4'b1111;
        endcase

endmodule
```

casez and casex

- casez
 - treats all z values in the case alternatives and the controlling expression as don't cares
- casex
 - treats all z and x values as don't cares

4-to-2 Priority Encoder

```

module priority (y, z, w);
  input [3 : 0] w;
  output [1 : 0] y;
  output z;
  reg [1 : 0] y;
  reg z;

  always @(w)
  begin
    z = 1;
    case (w)
      4'b1xxx: y = 3;
      4'b01xx: y = 2;
      4'b001x: y = 1;
      4'b0001: y = 0;
      default:
      begin
        z = 0;
        y = 2'bx;
      end
    endcase
  end


endmodule

```

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

The For Loop

 - Syntax—
for (initial_index; terminal_index; increment) statement;
- Examples—



```


module dec2to4 (y, w, en);

  input [1 : 0] w;
  input en;
  output [0 : 3] y;
  reg [0 : 3] y;
  integer k;

  always @(w or en)
    for (k = 0; k <= 3; k = k+1)
      if ((w == k) && (en == 1))
        y[k] = 1;
      else
        y[k] = 0;

endmodule

```

 

Priority Encoder

```
module priority (y, z, w);
  input [3 : 0] w;
  output [1 : 0] y;
  output z;
  reg [1 : 0] y;
  reg z;
  integer k;


  always @(w)
  begin
    Y = 2'bxx;
    z = 0;
    for ( k = 0; k < 4; k = k + 1 )
      if (w[k])
        begin
          y = k;
          z = 1;
        end
    end
  end
endmodule
```

w ₃	w ₂	w ₁	w ₀	y ₁	y ₀	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1



Verilog Operations (1/5)

Operator Type	Operator Symbols	Operation Perform
Bitwise	~	1 's complement
	&	Bitwise AND
		Bitwise OR
	^	Bitwise XOR
	~^ or ^~	Bitwise XNOR
Logical	!	NOT
	&&	AND
		OR

 

Verilog Operations (2/5)

Operator Type	Operator Symbols	Operation Perform
Reduction	&	Reduction AND
	~&	Reduction NAND
		Reduction OR
	~	Reduction NOR
	^	Reduction XOR
	~^ or ^~	Reduction XNOR
Arithmetic	+	Addition
	-	Subtraction
	-	2's complement
	*	Multiplication
	/	Division



Verilog Operations (3/5)

Operator Type	Operator Symbols	Operation Perform
Relational	>	Greater than
	<	Less than
	>=	Greater than or equal to
	<=	Less than or equal to
Equality	==	Logical equality
	!=	Logical inequality
Shift	>>	Right shift
	<<	Left shift
Concatenation	{}	Concatenation
Replication	{}	Replication
Conditional	?:	Conditional



Verilog Operations (4/5)

- Truth tables for bitwise operators

&	0	1	x
0	0	0	0
1	0	1	x
x	0	x	x

	0	1	x
0	0	1	x
1	1	1	1
x	x	1	x

^	0	1	x
0	0	1	x
1	1	0	x
x	x	x	x

~^	0	1	x
0	1	0	x
1	0	1	x
x	x	x	x



Verilog Operations (5/5)

Operator Type	Operator Symbols	Precedence
Complement	! ~ -	Highest precedence
Arithmetic	* / + -	
Shift	<< >>	
Relational	< <= > >=	
Equality	== !=	
Reduction	& ~& ^ ~^ ~	
Logical	&& 	
Conditional	?:	Lowest precedence



Tasks and Functions

■ Task

```

module mux16to1 (f, w, s16);
  input [0 : 15] w;
  input [3 : 0] s16;
  output f;
  reg f;

  always @(w or s16)
    case (s16[3:2])
      0: mux4to1 (w[0:3], s16[1:0], f);
      1: mux4to1 (w[4:7], s16[1:0], f);
      2: mux4to1 (w[8:11], s16[1:0], f);
      3: mux4to1 (w[12:15], s16[1:0], f);
    endcase

```

```

// Task that specifies a 4-to-1 multiplexer
task mux4to1;
  input [0:3] x;
  input [1:0] s4;
  output g;
  reg g;

  case (s4)
    0: g = x[0];
    1: g = x[1];
    2: g = x[2];
    3: g = x[3];
  endcase
endtask

endmodule

```



Tasks and Functions

■ Function

```

module mux16to1 (f, w, s16);
  input [0 : 15] w;
  input [3 : 0] s16;
  output f;
  reg f;

  // Function that specifies a 4-to-1 multiplexer
  function mux4to1;
    input [0 : 3] x;
    input [1 : 0] s4;

    case (s4)
      0: g = x[0];
      1: g = x[1];
      2: g = x[2];
      3: g = x[3];
    endcase
  endfunction

```

```

always @(w or s16)
  case (s16[3:2])
    0: mux4to1 (w[0:3], s16[1:0]);
    1: mux4to1 (w[4:7], s16[1:0]);
    2: mux4to1 (w[8:11], s16[1:0]);
    3: mux4to1 (w[12:15], s16[1:0]);
  endcase

endmodule

```



Gated D Latch

```
module d_latch (q, d, clk);  
  
  input d, clk;  
  output q;  
  reg q;  
  
  always @(q or clk)  
    if (clk)  
      q = d;  
  
endmodule
```



D Flip-Flop

```
module flipflop (q, d, clk);  
  input d, clk;  
  output q;  
  reg q;  
  
  always @(posedge clk)  
    q = d;  
  
endmodule
```


Blocking (Procedural) Assignment vs. Non-Blocking (Concurrent) Assignment

Blocking assignment

```
always @(x)
begin
  count = 0;
  for (k = 0; k < n; k = k + 1)
    count = count + x[k];
end
```



```
count = 0 + x[0];
count = x[0] + x[1];
count = x[1] + x[2];
```

Non-blocking assignment

```
always @(x)
begin
  count = 0;
  for (k = 0; k < n; k = k + 1)
    count <= count + x[k];
end
```



```
count = 0 + x[0];
count = 0 + x[1];
count = 0 + x[2];
```

Two Parallel Flip-Flops


■ Blocking (procedural) assignment

```
module example7_3 (q1, q2, d, clk);
```

```
  input d, clk;
  output q1, q2;
  reg q1, q2;
```

```
  always @(posedge clk)
  begin
    q1 = d;
    q2 = q1;
  end
```


```
endmodule
```

 

Two Cascaded Flip-Flops


- Non-blocking (concurrent) assignment
 
```
module example(q1, q2, d, clk);  
  input d, clk;  
  output q1, q2;  
  reg q1, q2;  
  
  always @(posedge clk)  
  begin  
    q1 <= d;  
    q2 <= q1;  
  end  
endmodule
```



Example for Blocking (Procedural) Assignment

```
module example(f, g, x1, x2, x3, clk);  
  input x1, x2, x3, clk;  
  output f, g;  
  reg f, g;  
  
  always @(posedge clk)  
  begin  
    f = x1 & x2;  
    g = f | x3;  
  end  
endmodule
```

 

Example for Non-Blocking (Concurrent) Assignment

```
module example (f, g, x1, x2, x3, clk);
```

```
  input x1, x2, x3, clk;
  output f, g;
```

```
  reg f, g;
```


```
  always @(posedge clk)
  begin
```

```
    f <= x1 & x2;
```

```
    g <= f | x3;
```

```
  end
```

```
endmodule
```

 

n-Bit Register

Synchronous Reset

```
module regn (q, d, clk, rst_n);
```

```
  parameter N = 16;
```

```
  input clk, rst_n;
```

```
  input [N - 1 : 0] d;
```

```
  output [N - 1 : 0] q;
```

```
  reg [N - 1 : 0] q;
```

```
  always @(posedge clk)
```

```
  if(!rst_n)
```

```
    q <= 0;
```

```
  else
```

```
    q <= d;
```

```
endmodule
```

Asynchronous Reset

```
module regn (q, d, clk, rst_n);
```

```
  parameter N = 16;
```

```
  input clk, rst_n;
```

```
  input [N - 1 : 0] d;
```

```
  output [N - 1 : 0] q;
```

```
  reg [N - 1 : 0] q;
```

```
  always @(negedge rst_n or posedge clk)
```

```
  if(!rst_n)
```


```
    q <= 0;
```

```
  else
```

```
    q <= d;
```

```
endmodule
```

Moore-Type Finite State Machine

 


Chuen-Yau Chen

```

module moore (z, clk, w, rst_n);
  input clk, w, rst_n;
  output z;
  reg [1:0] y;
  parameter [1:0] a = 2'b00, b = 2'b01, c = 2'b10;

  always @(w or y)
  begin
    case (y)
      a: if (w == 0) y = a;
         else y = b;
      b: if (w == 0) y = a;
         else y = c;
      c: if (w == 0) y = a;
         else y = c;
      default: y = 2'bxx;
    endcase
  end
  always @(posedge clk or negedge rst_n)
  begin
    if (rst_n == 0)
      y <= a;
    else
      y <= y;
    end
    assign z = (y == c)
  end
endmodule
  
```

Moore-Type Finite State Machine

 

Chuen-Yau Chen

```


module moore (z, clk, w, rst_n);
  input clk, w, rst_n;
  output z;
  reg [1:0] state, next_state;
  parameter [1:0] a = 2'b00, b = 2'b01, c = 2'b10;

  always @(posedge clk or negedge rst_n)
  if (rst_n == 0)
    state <= a;
  else
    state <= next_state;

  always @(posedge clk or negedge rst_n)
  begin
    if (rst_n == 0)
      next_state <= a;
    else
      case (y)
        a: if (w == 0) next_state <= a;
           else next_state <= b;
        b: if (w == 0) next_state <= a;
           else next_state <= c;
        c: if (w == 0) next_state <= a;
           else next_state <= c;
        default: next_state <= 2'bxx;
      endcase
    end
  end

  assign z = (y == c);
endmodule
  
```

Mealy-Type FSM

 

```

module mealy (z, clk, w, rst_n);

  input clk, w, rst_n;
  output z;
  reg [1:0] state, next_state;
  parameter a = 0, b = 1;

  always @(posedge clk or negedge rst_n)
    if (rst_n == 0)
      state <= a;
    else
      state <= next_state;

  always @(w or state)
    begin
      case (state)
        a: if (w == 0)
          begin
            next_state = a; z = 0;
          end
        else
          begin
            next_state = b; z = 0;
          end
      endcase
    end
  
```

```

    b: if (w == 0)
      begin
        y = a;
        z = 0;
      end
    else
      begin
        y = b;
        z = 1;
      end
    endcase
  
```

endmodule

57

How to Generate Clock Signal in Testbenches?

```

initial
  begin
    clk = 1'b0;
    #5
    clk = 1'b1;
    #5
    clk = 1'b0;
    #5
    clk = 1'b1;
    $finish;
  end
  
```

```

initial
  begin
    clk = 1'b0;
    #20
    $finish;
  end
  always
    #5 clk = ~clk;
  
```



58

Formal and Actual Names for Port Association by Name

```
module fulladd (cout, s, cin, x, y); ← formal_name
  input cin, x, y;
  output cout, s;

  assign s = x ^ y ^ cin;
  assign cout = (x & y) | (x & cin) | (y & cin);
endmodule
```

```
module adder4 (carryout, s, carryin, x, y); ← actual_name
  input carryin;
  input [3:0] x, y;
  output [3:0] s;
  output carryout;
  wire [3:1] c;


  fulladd stage0 (c[1], s[0], carryin, x[0], y[0]);
  fulladd stage1 (c[2], s[1], c[1], x[1], y[1]);
  fulladd stage2 (c[3], s[2], c[2], x[2], y[2]);
  fulladd stage3 (carryout, s[3], c[3], x[3], y[3]);
endmodule
```

.formal name (actual name)

(.cout (c[1]), .s (c[0]), .cin (carryin),
.x (x[0]), .y (y[0]))

always Blocks
 
```
always @(sensitivity_list)
  [begin]
    [procedural assignment statements]
    [if-else statements]
    [case statements]
    [for loops]
    [task and function calls]
  [end]
```



References / Sources

- Charles H. Roth, Jr., Larry L Kinney, *Fundamentals of Logic Design*, 7th Ed., Cengage Learning , 2014. (ISBN-13: 978-0-13-246557-1)
- Samir Palnitkar, *Verilog HDL*, 2nd. Ed., Prentice Hall, 2003. (ISBN-13: 978-0-13-259970-2)
- Michael D. Ciletti, *Advanced Digital Design with the Verilog HDL*, 2nd Ed., Prentice Hall, 2010. (ISBN-13: 978-0-13-246557-1)